



NORTH SOUTH UNIVERSITY
DEPARTMENT OF ELECTRICAL & COMPUTER
ENGINEERING

Assignment-1


Summer 2025

EEE141: Electrical Circuits I

Section: 15


Name: Nadim Mahmud
ID: 1921877642

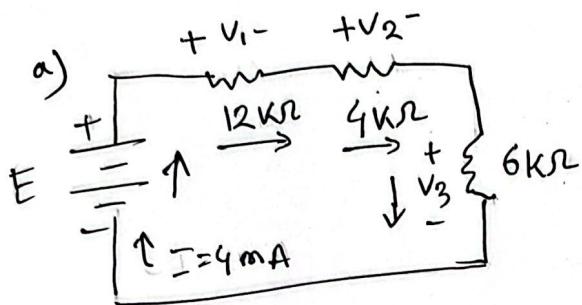1. Find the applied voltage E necessary to develop the current specified in each circuit.



$$\text{here, } R_T = R_1 + R_2 + R_3 \\ = 22 \text{ k}\Omega$$
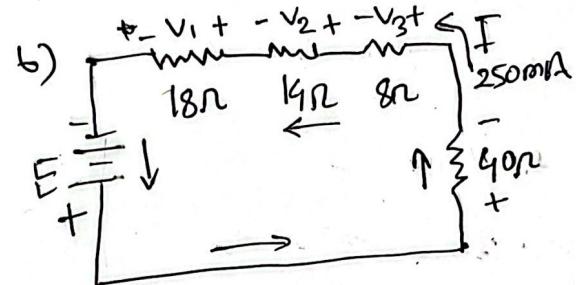
$$E = IR_T \\ = 4 \text{ mA} \times 22 \text{ k}\Omega \\ = 88 \text{ V}$$




$$\text{here, } R_T = 18 + 14 + 8 + 40 \\ = 80 \Omega$$

$$E = IR_T \\ = 250 \text{ mA} \times 80 \Omega \\ = 20 \text{ V}$$

Ans.

2. Using the information provided, find the un-known quantities.

a)

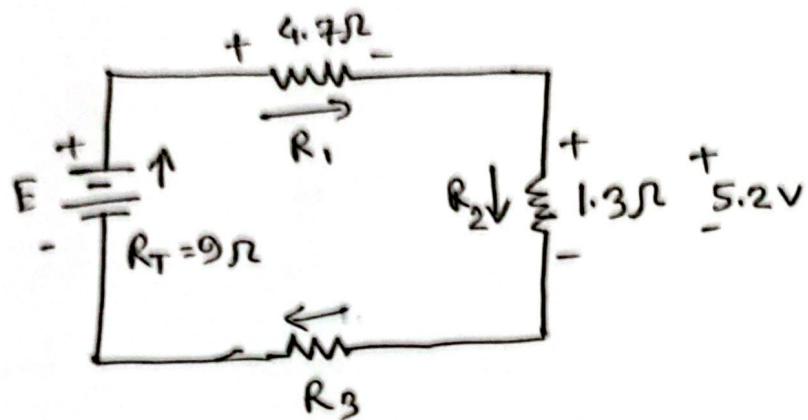

$$R_3 = R_T - (R_1 + R_2)$$

$$= 9 - 6$$

$$= 3$$

$$\text{Current } I = \frac{V_2}{R_2}$$

$$= 4 \text{ A}$$

$$\text{Voltage } V_1 = IR_1$$

$$= 4 \times 4.7$$

$$= 18.8 \text{ V}$$


$$V_2 = 5.2 \text{ V}$$

$$V_3 = IR_3$$

$$= 12 \text{ V}$$

Ans.

b.

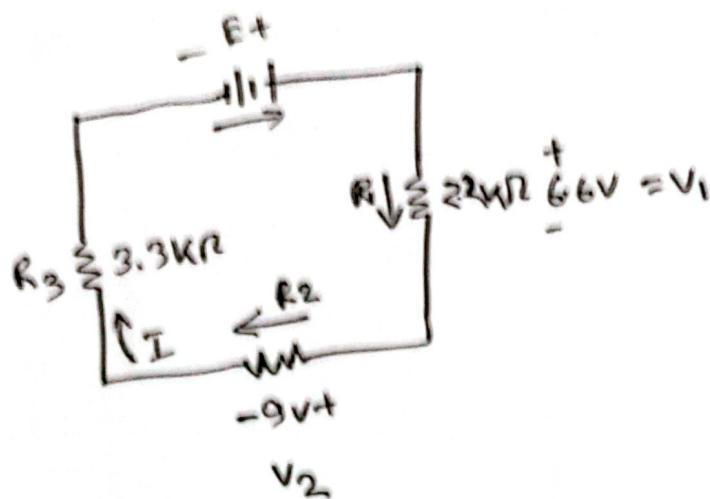

$$\text{Current } I = \frac{V_1}{R_1}$$

$$= 3\text{ mA}$$

$$\text{Resistance } R_2 = \frac{V_2}{I}$$

$$= 3\text{ k}\Omega$$

$$TR = R_1 + R_2 + R_3$$

$$= 2.2 + 3 + 3.3$$


$$= 8.5\text{ k}\Omega$$

$$\begin{aligned} \text{Total voltage } E &= IR \\ &= 3\text{ mA} \times 8.5\text{ k}\Omega \\ &= 25.5\text{ V} \end{aligned}$$

$$\begin{aligned} \text{Voltage } V_3 &= IR_3 \\ &= 3 \times 3.3 \\ &= 9.9\text{ V} \end{aligned}$$

Ans.

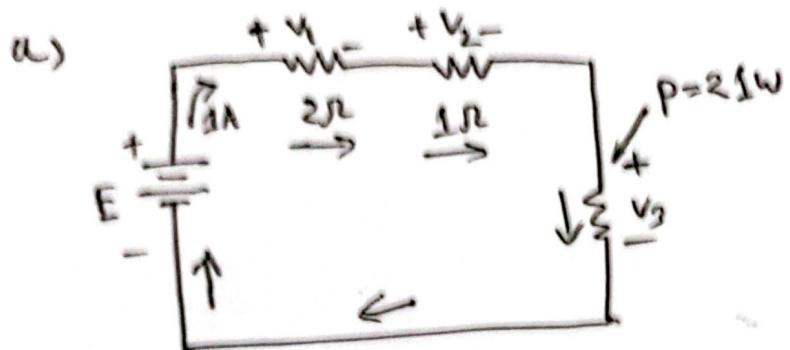3. Using the information provided, find the unknown quantities.



$$\text{Power in } P_3 = I^2 R_3$$

$$\begin{aligned} R_3 &= \frac{P_3}{I^2} \\ &= \frac{21W}{1A} \\ &= 21\Omega \end{aligned}$$

$$\begin{aligned} R_T &= (2 + 1 + 21)\Omega \\ &= 24\Omega \end{aligned}$$


$$\begin{aligned} \text{Voltage } E &= IR_T \\ &= 24V \end{aligned}$$

$$V_1 = IR_1 = 2V$$

$$V_2 = 1V$$

$$V_3 = 21V$$

Ans.

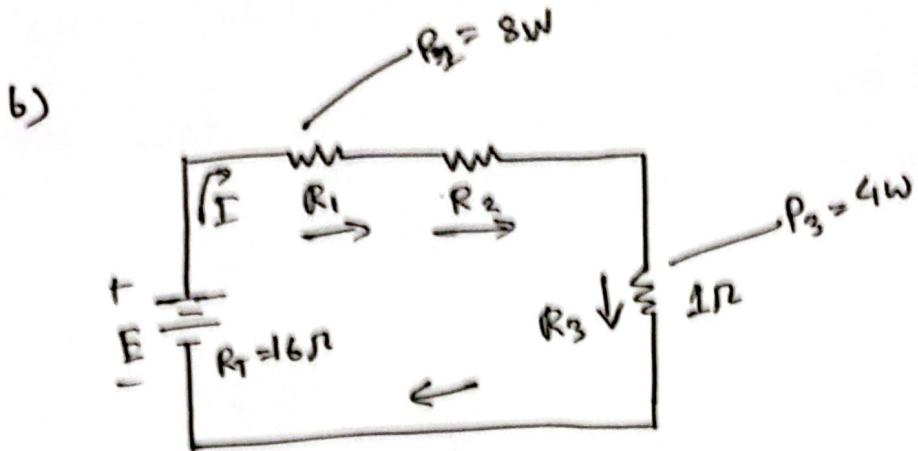

current

$$P_3 = I^2 R_3$$

$$I = \sqrt{\frac{P_3}{R_3}}$$

$$= 2A$$

resistance $R_1 = \frac{P_1}{I^2} = \frac{8}{2^2} = 4\Omega$

$$\begin{aligned} R_2 &= R_T - (R_1 + R_3) \\ &= 16 - 5 \\ &= 11\Omega \end{aligned}$$

voltage IR_T

$$= 32V$$

$$V_1 = IR_1 = 2 \times 4 = 8V$$

$$V_2 = 2 \times 11 = 22V$$

$$V_3 = 2V$$


An.

4. Determine the current I and its direction

for each network. Before solving for I ,

reduce each network with a single voltage

source.

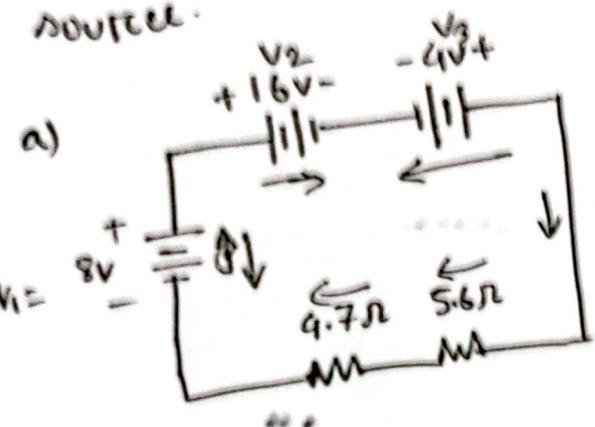

Combine the voltage

$$E = -V_1 + V_2 - V_3$$

$$= -8 + 16 - 4$$

$$= 4 \text{ V}$$

$$R_T = R_1 + R_2$$


$$= 10.3 \Omega$$

$$\text{Current } I = \frac{E}{R_T}$$

$$= \frac{4}{10.3}$$

$$= 0.388 \text{ A}$$

A-

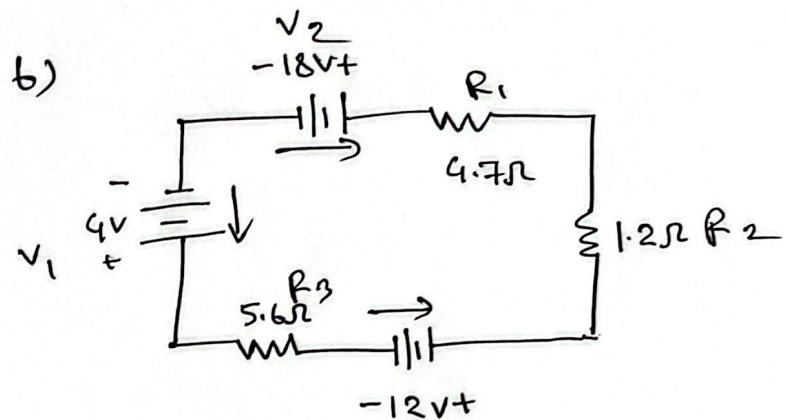

$$E = +4 - 18 - 12$$

$$= -2 \text{ V}$$

$E = 2 \text{ V}$ (If we change the direction)

$$R_T = R_1 + R_2 + R_3$$

$$= 11.5 \Omega$$


Current $I = \frac{E}{R_T}$

$$= \frac{2}{11.5}$$

$$= 0.17 \text{ A}$$

Au.

5. Using KVL, find the unknown voltage.

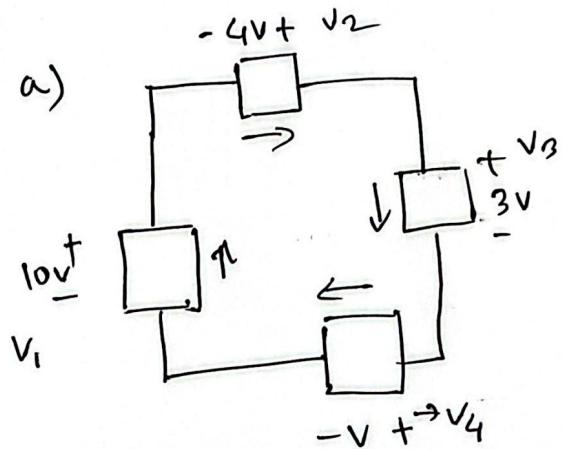


Using KVL

$$v_1 + v_2 + v_3 + v_4 = 0$$

$$-10 - 4 + 3 + v_4 = 0$$

$$-11 + v_4 = 0$$

$$v_4 = 11$$

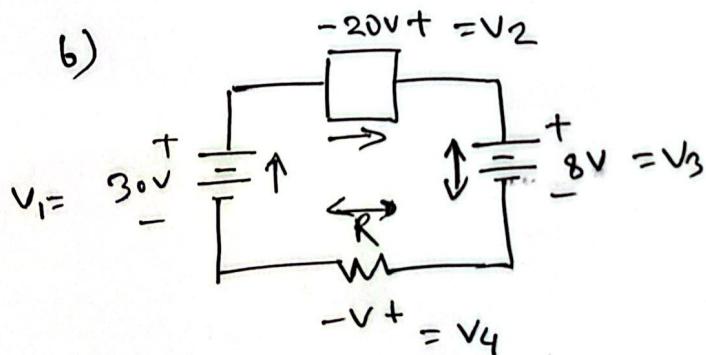


$$v_1 + v_2 + v_3 + v_4 = 0$$

$$-30 - 20 + 8 + v_4 = 0$$

$$-42 + v_4 = 0$$

$$v_4 = 42$$

An.

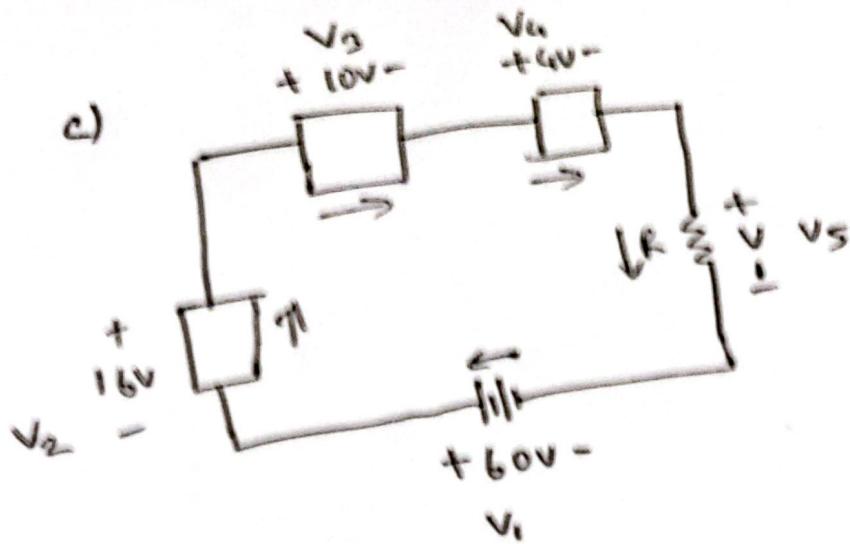

Using KVL

$$V_1 + V_2 + V_3 + V_4 + V_5 = 0$$

$$-60 - 16 + 10 + 4 + V_5 = 0$$


$$-62 + V_5 = 0$$

$$V_5 = 62$$

here unknown voltage $V = 62$

Ans.


6. Using KVL, Find the unknown Voltage.

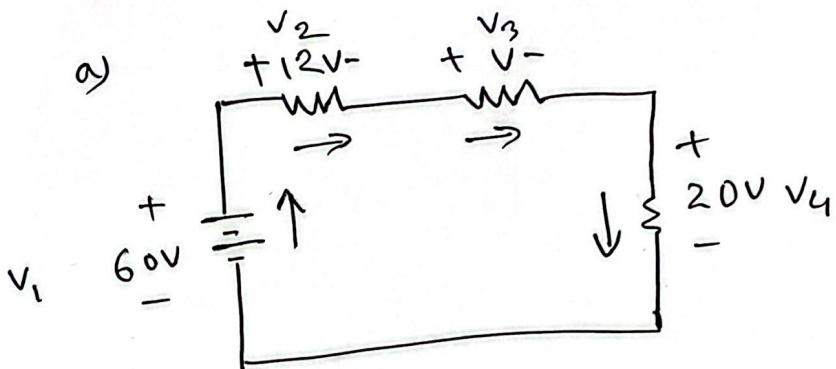

$$v_1 + v_2 + v_3 + v_4 = 0$$

$$-60 + 12 + v_3 + 20 = 0$$

$$v_3 = 28 \text{ V} \leftarrow$$

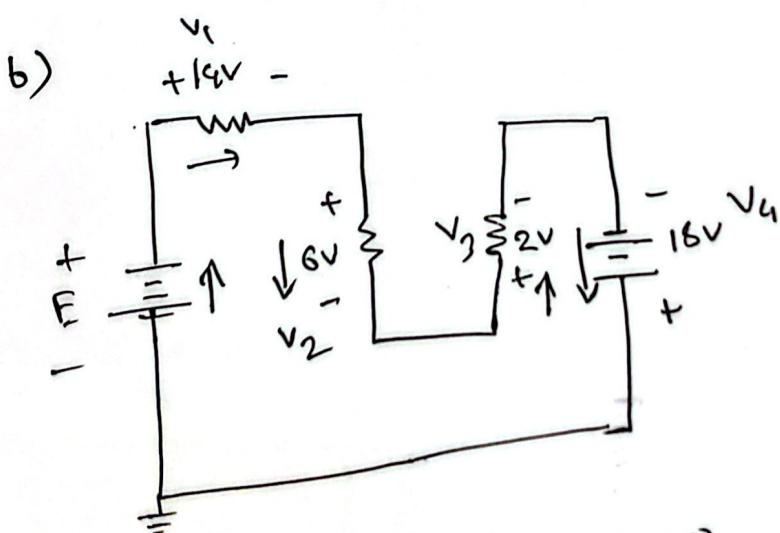

$$E + v_1 + v_2 + v_3 + v_4 = 0$$


$$-E + 14 + 6 + 2 - 18 = 0$$

$$-E + 4 = 0$$

$$\underline{E} = 4 \text{ V}$$

A

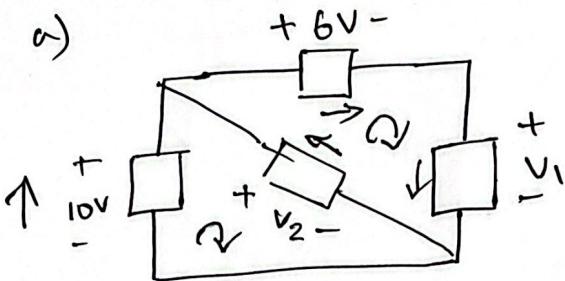
7. Using KVL, find the unknown voltage v_1 and v_2 .



$$\text{1st loop} \\ -10 + v_2 = 0 \\ v_2 = 10 \text{ V}$$

$$\text{2nd loop} \\ -10 + 6 + v_1 = 0 \\ v_1 = 4 \text{ V}$$

b)

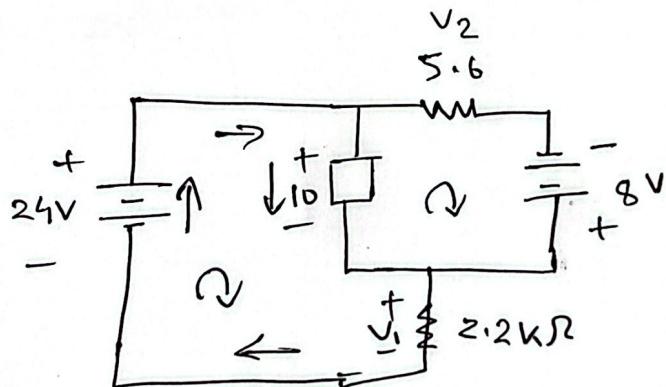

1st loop,

$$-24 + 10 + v_1 = 0$$

$$v_1 = 14 \text{ V}$$


2nd loop,

$$-10 + v_2 - 8 = 0$$

$$v_2 = 18 \text{ V}$$

Ans.

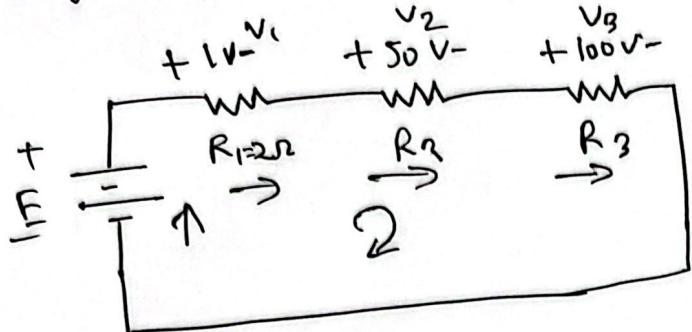9. Using VDR, find the indicated resistances.



here current,

$$I = \frac{V}{R_1} = \frac{1}{2} = 0.5A$$

~~resistances~~

$$\begin{aligned} R_1 &= 2\Omega \\ R_2 &= 25\Omega \\ R_3 &= I \times V_3 = 50\Omega \end{aligned}$$

using KVL we get value of E


$$-E + 1 + 50 + 100 = 0$$

$$E = 151V$$

using
VDR

$$\begin{aligned} R_2 &= \frac{V_2 \times R_T}{E} \\ R_2 &= \frac{50 \times (R_1 + R_2 + R_3)}{151} \\ R_2 &= \frac{100 + 50R_2 + 50R_3}{151} \end{aligned}$$

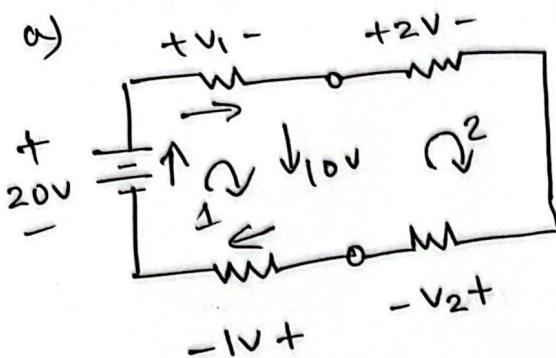8. Using KVL, Find the voltage v_1 and v_2




Int loop,

$$-20 + v_1 + 10 + 1 = 0$$

$$-9 + v_1 = 0$$

$$v_1 = 9V$$

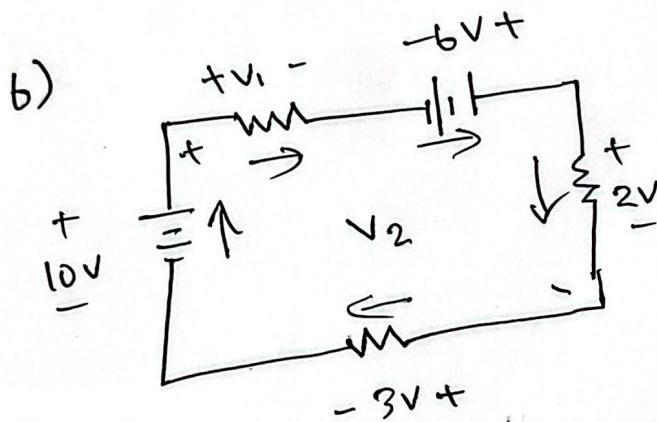

$$-10 + v_2 + 3 = 0$$

$$-7 + v_2 = 0$$

$$v_2 = 7V$$

$$-10 + v_1 - 6 + 2 + 3 = 0$$

$$-11 + v_1 = 0$$

$$v_1 = 11V$$

Ans

using VDR

$$V_1 = R_1 \frac{E}{R_T}$$

$$I = 2 \frac{151}{R_T}$$

$$\frac{302}{R_T} = 1$$

$$302 = R_T$$

$$V_2 = \frac{R_2 E}{R_T}$$

$$R_2 = \frac{V_2 R_T}{E}$$

$$= \frac{50 \times 302}{151}$$

$$= 100 \Omega$$


$$V_3 = \frac{R_3 E}{R_T}$$

$$R_3 = \frac{100 \times 302}{151}$$

$$= 200 \Omega$$

An.

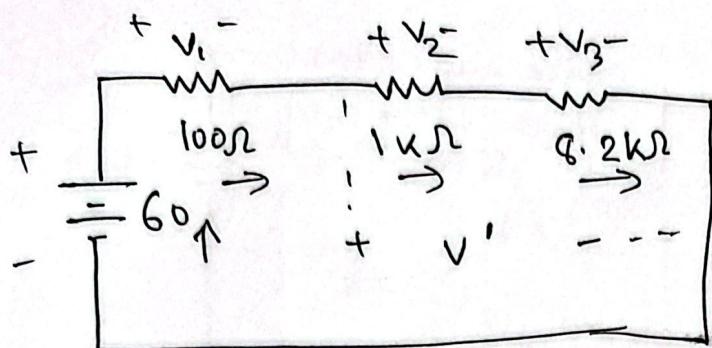10. Using VDR, find the indicated voltage.



Using VDR,

$$R_T = 100\Omega + 1k\Omega + 8.2k\Omega$$

$$= 9.3k\Omega$$

$$V_1 = \frac{R_1 \times E}{R_T}$$

$$= \frac{100\Omega \times 60V}{9.3k\Omega}$$

$$= 0.65V$$

$$V_2 = \frac{R_2 \times E}{R_T}$$

$$= 6.45V$$

$$V_0' = \frac{E \times R'}{R_T}$$

$$= \frac{E \times (R_2 + R_3)}{R_T}$$

$$= \frac{60 \times 9.2}{9.3}$$

$$= 59.35V$$


$$V_3 = \frac{R_3 \times E}{R_T}$$

$$= 52.90V$$

An.

II. Using the VDR, find the indicated voltages.

a)

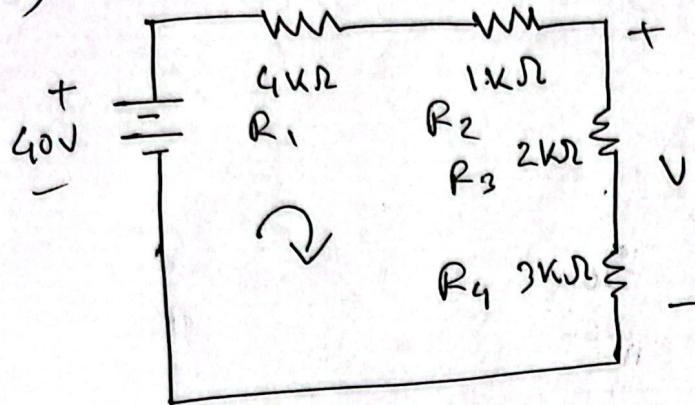

$$R_T = 4 + 1 + 2 + 3 = 10 \text{ k}\Omega$$


$$V' = \frac{ER'}{R_T}$$

$$= \frac{40(R_3 + R_4)}{10}$$

$$= \frac{200}{10}$$

$$= 20 \text{ V}$$

b)

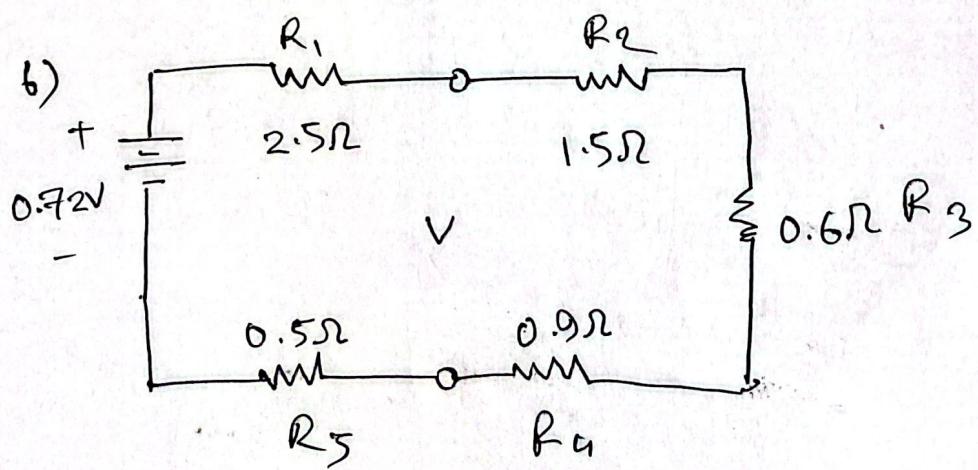


$$R_T = 2.5 + 1.5 + 0.6 + 0.9 + 0.5 \\ = 6 \Omega$$

$$V' = \frac{ER'}{R_T} \\ = \frac{0.72(R_2 + R_3 + R_4)}{6} \\ = \frac{0.72 \times 3}{6}$$

$$V = 0.36 V$$

An.

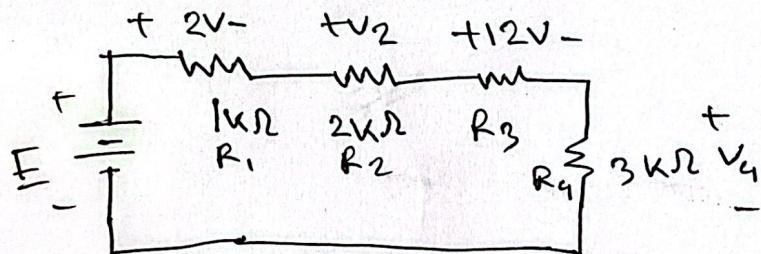12. Using the information, find the unknown values.



$$\text{Current} = I \times R_1 = 2 \times 1k\Omega = 2mA \quad | \quad R_3 = \frac{V_3}{I}$$

$$V_2 = 2 \times 2 = 4V$$

$$V_4 = 3 \times 2 = 6V$$

$$= \frac{12}{2mA}$$


$$= 6k\Omega$$

$$\text{Using KVL} \quad -E + 2 + 4 + 12 + 6 = 0 \\ -E + 24 = 0$$

An.

$$E = 24 V$$

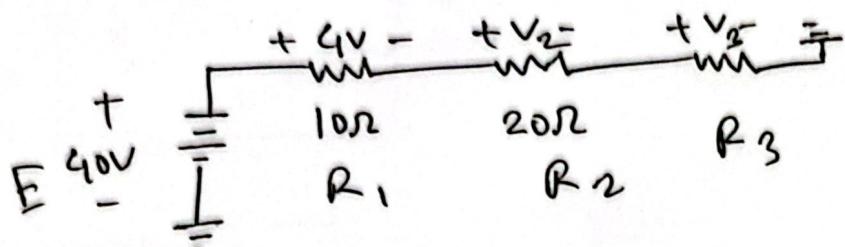13. Using the information provided, find the unknown quantities.



$$\text{current } I = \frac{V}{R} = \frac{9}{10} = 0.9 \text{ A}$$

$$\text{voltage } V_1 = 4 \text{ V}$$

$$V_2 = \cancel{10} 8 \text{ V}$$

$$\text{using KVL } -9 + 4 + \cancel{8} + V_3 = 0$$

$$V_3 = 2 \text{ V}$$

Resistance,

$$R_3 = \frac{V_3}{I}$$


$$= \frac{2}{0.9} \rightarrow 0.9$$

$$= 52 \Omega$$

$$= 70 \Omega$$

An.

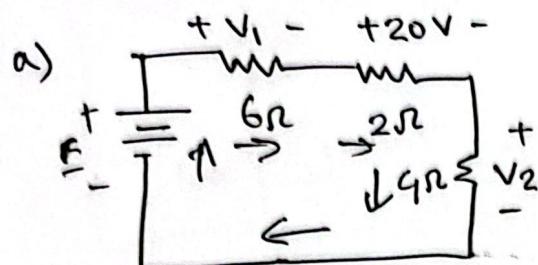19. Using VDR or KVL, to find unknown voltage



$$\text{current } I = \frac{V_2}{R_2} = \frac{20}{2} = 10A$$


$$V_1 = 6 \times 10 = 60V$$

$$V_2 = 4 \times 10 = 40V$$

Using KVL $-E + V_1 + 20V + 40V = 0$

$$E = 120V$$

b)

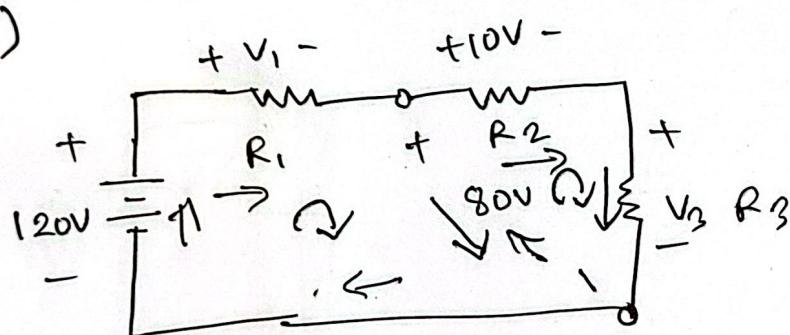


$$\text{KVL}, -120 + V_1 + 80 = 0$$

$$V_1 = 40V$$

$$-80 + 10 + V_3 = 0$$

$$V_3 = 70V$$

An.

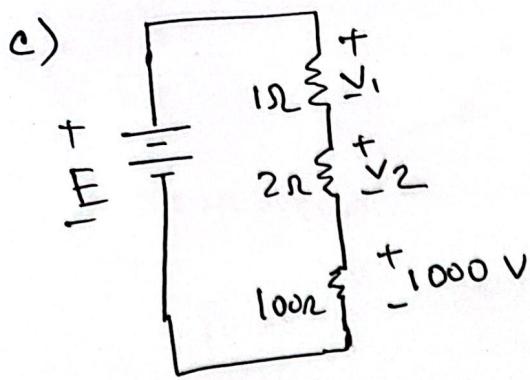

$$\text{current } I = 10 \text{ A}$$

$$\text{voltage } v_2 = 20 \text{ V}$$


$$v_1 = 10 \text{ V}$$

$$\text{Using KVL} \quad -E + \frac{10}{100} + 20 + 1000 = 0$$

$$-E + 1030 = 0$$

$$E = 1030 \text{ V}$$

d)

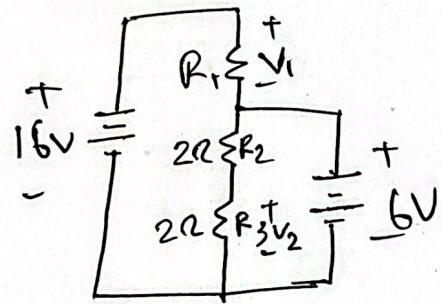

$$v_2 = \frac{ER}{R_T}$$

$$\text{KVL} \quad -16 + v_1 + 6 = 0$$


$$v_1 = 10 \text{ V}$$

$$= \frac{6 \cdot 2}{4}$$

$$= 3 \text{ V}$$

An.

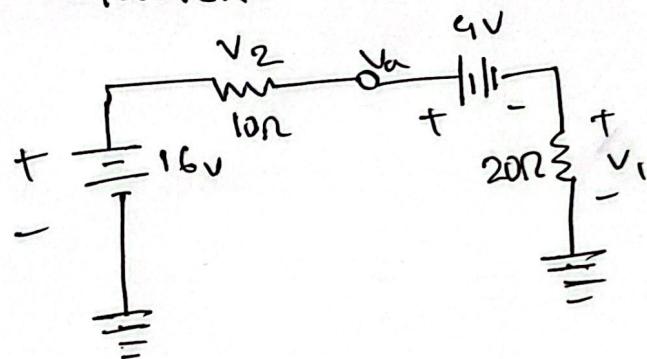15. Determine the voltage v_a and v_i for the networks



$$\text{current } I = \frac{\text{Total Voltage}}{\text{Total Resistance}}$$

$$= 0.4$$

$$v_2 = 10 \times 0.4$$

$$= 4V$$

$$v_a = 16 - 4$$


$$= 12V$$

$$v_i = 20 \times 0.4$$

$$= 8V$$

Aw:

6)

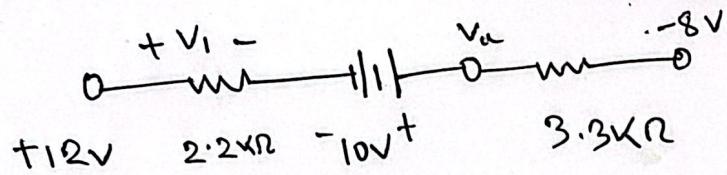

$$\text{Current } I = \frac{30\text{ V}}{5.5\text{ k}\Omega} = 5.45 \text{ mA}$$

$$V_1 = IR_1 = 2.2 \times 5.45 \\ = 12\text{ V}$$

$$V_o = 12 - 12 + 10 \\ = 10\text{ V}$$


Ans.

16. For the network in fig. determine the voltage.

a) V_a, V_b, V_c, V_d, V_e

b) V_{ab}, V_{dc}, V_{cb}

c) V_{ae}, V_{db}

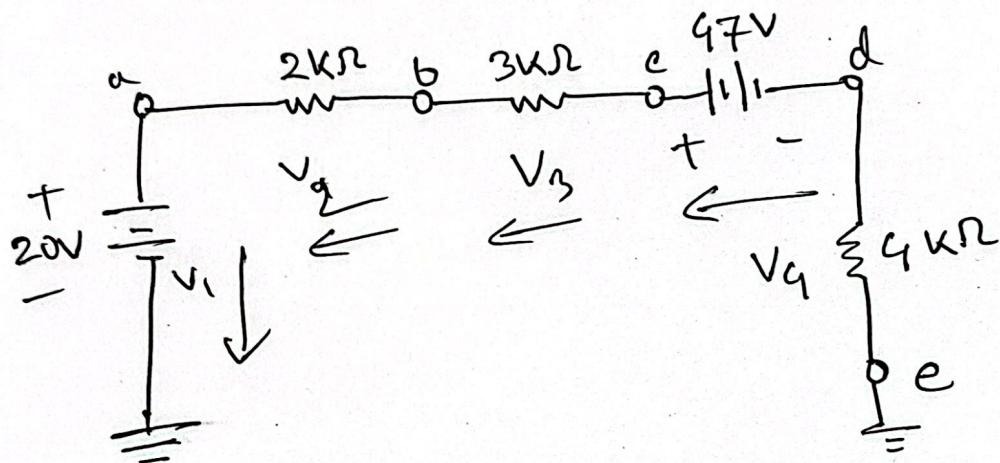

Current $I = \frac{\text{Total voltage}}{R_T}$

$$= \frac{27}{9} = 3mA$$

$$V_2 = 6V$$

$$V_3 = 9V$$

$$V_4 = 12V$$

$$V_{ab} = -38V$$

$$V_a = 20V$$

$$V_b = 26V$$

$$V_c = 35V$$

$$V_d = 35 - 47 = -12V$$

$$V_e = 0V$$

$$V_{ab} = -6V$$

$$V_{dc} = -47$$

$$V_{cb} = 9V$$


$$V_{ae} = -15V$$

17. For the network fig. determine the voltage.

a) V_a, V_b, V_c, V_d

b) V_{ab}, V_{cb}, V_{cd}

c) V_{ad}, V_{ca}

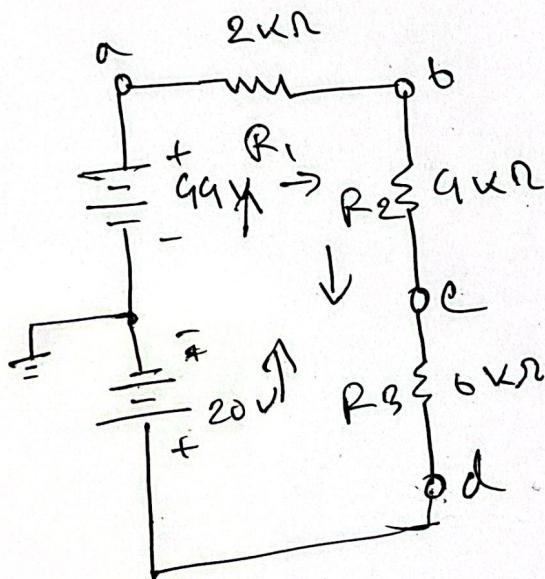

Given Current $I = \frac{24}{12} = 2 \text{ mA}$

$V_{R_1} = 2 \times 2 = 4 \text{ V}$

$V_{R_2} = 8 \text{ V}$

$V_{R_3} = 12 \text{ V}$

a) $V_a = 49 \text{ V}$
 $V_b = 49 - 4 = 45 \text{ V}$
 $V_c = 49 - 4 - 8 = 37 \text{ V}$
 $V_d = 20 \text{ V}$

b) $V_{ab} = 4 \text{ V}$
 $V_{cb} = -8 \text{ V}$
 $V_{cd} = 12 \text{ V}$

c) $V_{ad} = V_b - V_d$
 $= 24 \text{ V}$

$V_{ca} = -12 \text{ V}$

Ans.